
Assignment 01

Make Logic Gates

Content

- | | |
|---------|---------|
| 1. AND | 5. NOR |
| 2. OR | 6. XOR |
| 3. NOT | 7. XNOR |
| 4. NAND | |

AND Gate

AND Gate

AND Gate



2-input AND Gate

Truth Table


B	A	Q
0	0	0
0	1	0
1	0	0
1	1	1

AND Gate in Console

```
iverilog -o f_and.vvp f_and_tb.v f_and.v
iverilog -o f_and.vvp f_and_tb.v f_and.v
Process started (PID=136000) >>>
<<< Process finished (PID=136000). (Exit code 0)
===== READY =====

vvp f_and.vvp
vvp f_and.vvp
Process started (PID=135532) >>>
VCD info: dumpfile f_and.vcd opened for output.
time    B      A      Q
0:      0      0      0
10:     0      1      0
20:     1      0      0
30:     1      1      1
<<< Process finished (PID=135532). (Exit code 0)
===== READY =====
```


AND Gate in gtkwave

 

OR Gate

OR Gate

OR Gate

 

2-input OR Gate


Truth Table

B	A	Q
0	0	0
0	1	1
1	0	1
1	1	1

OR Gate in Console

```
liverilog -o f_or.vvp f_or_tb.v f_or.v
liverilog -o f_or.vvp f_or_tb.v f_or.v
Process started (PID=122176) >>>
<<< Process finished (PID=122176). (Exit code 0)
===== READY =====
vvp f_or.vvp
vvp f_or.vvp
Process started (PID=127876) >>>
VCD info: dumpfile f_or.vcd opened for output.
time    B    A    Q
0:      0    0    0
10:     0    1    1
20:     1    0    1
30:     1    1    1
<<< Process finished (PID=127876). (Exit code 0)
===== READY =====
```


OR Gate in gtkwave

 

NOT Gate

NOT Gate

NOT Gate

 

Inverter or NOT Gate


Truth Table

A	Q
0	1
1	0

NOT Gate in Console

```
iverilog -o f_not.vvp f_not_tb.v f_not.v
iverilog -o f_not.vvp f_not_tb.v f_not.v
Process started (PID=128984) >>>
<<< Process finished (PID=128984). (Exit code 0)
===== READY =====
vvp f_not.vvp
vvp f_not.vvp
Process started (PID=130320) >>>
VCD info: dumpfile f_not.vcd opened for output.
time    A    Q
0:      0    1
10:     1    0
<<< Process finished (PID=130320). (Exit code 0)
===== READY =====
```

NOT Gate in gtkwave

 

NAND Gate

NAND Gate

NAND Gate



2-input NAND Gate


Truth Table

B	A	Q
0	0	1
0	1	1
1	0	1
1	1	0

NAND Gate in Console

```
iverilog -o f_nand.vvp f_nand_tb.v f_nand.v
iverilog -o f_nand.vvp f_nand_tb.v f_nand.v
Process started (PID=136712) >>>
<<< Process finished (PID=136712). (Exit code 0)
===== READY =====
vvp f_nand.vvp
vvp f_nand.vvp
Process started (PID=122148) >>>
VCD info: dumpfile f_nand.vcd opened for output.
time    B    A    Q
0:      0    0    1
10:     0    1    1
20:     1    0    1
30:     1    1    0
<<< Process finished (PID=122148). (Exit code 0)
===== READY =====
```


NAND Gate in gtkwave

 

NOR Gate

NOR Gate

NOR Gate

 

2-input NOR Gate


Truth Table

B	A	Q
0	0	1
0	1	0
1	0	0
1	1	0

NOR Gate in Console

```
iverilog -o f_nor.vvp f_nor_tb.v f_nor.v
iverilog -o f_nor.vvp f_nor_tb.v f_nor.v
Process started (PID=122984) >>>
<<< Process finished (PID=122984). (Exit code 0)
===== READY =====
vvp f_nor.vvp
vvp f_nor.vvp
Process started (PID=131152) >>>
VCD info: dumpfile f_nor.vcd opened for output.
time    B    A    Q
0:      0    0    1
10:     0    1    0
20:     1    0    0
30:     1    1    0
<<< Process finished (PID=131152). (Exit code 0)
===== READY =====
```


NOR Gate in gtkwave

 

XOR Gate

XOR Gate

XOR Gate

 


2-input Ex-OR Gate

Truth Table		
B	A	Q
0	0	0
0	1	1
1	0	1
1	1	0

XOR Gate in Console

```
iverilog -o f_xor.vvp f_xor_tb.v f_xor.v
iverilog -o f_xor.vvp f_xor_tb.v f_xor.v
Process started (PID=136356) >>>
<<< Process finished (PID=136356). (Exit code 0)
===== READY =====
vvp f_xor.vvp
vvp f_xor.vvp
Process started (PID=136936) >>>
VCD info: dumpfile f_xor.vcd opened for output.
time    B    A    Q
0:      0    0    0
10:     0    1    1
20:     1    0    1
30:     1    1    0
<<< Process finished (PID=136936). (Exit code 0)
===== READY =====
```


XOR Gate in gtkwave

 

XNOR Gate

XNOR Gate

XNOR Gate

 

2-input Ex-NOR Gate

Truth Table

B	A	Q
0	0	1
0	1	0
1	0	0
1	1	1

XNOR Gate in Console

```
iverilog -o f_xnor.vvp f_xnor_tb.v f_xnor.v
iverilog -o f_xnor.vvp f_xnor_tb.v f_xnor.v
Process started (PID=128696) >>>
<<< Process finished (PID=128696). (Exit code 0)
===== READY =====
vvp f_xnor.vvp
vvp f_xnor.vvp
Process started (PID=133408) >>>
VCD info: dumpfile f_xnor.vcd opened for output.
time    B      A      Q
0:      0      0      1
10:     0      1      0
20:     1      0      0
30:     1      1      1
<<< Process finished (PID=133408). (Exit code 0)
===== READY =====
```

XNOR Gate in gtkwave

